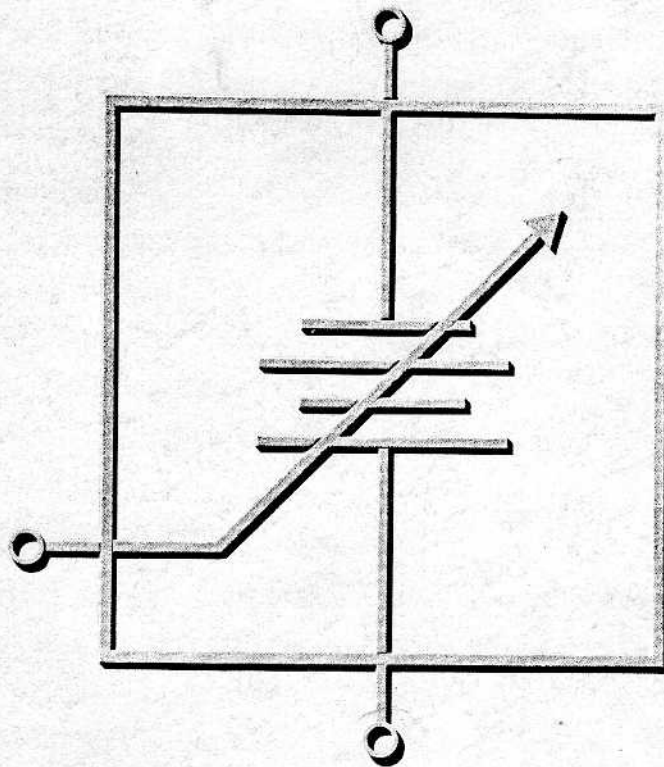


**$\mu$ A723**  
**PRECISION**  
**VOLTAGE**  
**REGULATOR**

4/15



**Application Notes**

**FAIRCHILD**  
SEMICONDUCTOR

## TABLE OF CONTENTS

	Page
Circuit Building Blocks for Voltage Regulators - Michael M. Scott . . . . .	1.1
A New Versatile Precision Voltage Regulator - J. Darryl Lieux . . . . .	2.1
Linear Voltage Regulators Using a New Monolithic Circuit - Robert D. Ricks . . . . .	3.1
Switching Regulator Design Using The $\mu$ A723 Precision Voltage Regulator - Michael J. English . . . . .	4.1

## ACKNOWLEDGEMENTS

The authors wish to gratefully acknowledge the contributions of Jim Giles and Murray Siegel for technical assistance, Johan Lund and Larry Stenger for process development and manufacturing of developmental units, Bob Sleeth and Don Lewis for computer programming, data processing, and automatic tester design, and Gail Short and Kay George for typing the manuscripts.

## CIRCUIT BUILDING BLOCKS FOR VOLTAGE REGULATORS

by Michael M. Scott

Today the engineer who must decide to buy out or build a power supply is faced with an impressive array of choices. He may buy complete power supplies from many vendors or build a supply using commercially available modules, hybrids or monolithic voltage regulators. He may even decide to design it himself with discrete components and integrated circuit op amps. Voltage regulators consist of basic building blocks shown in Figure 1. The goal is to assemble the blocks to get the typical "ideal" regulator (figure 2).


Ignoring biasing and current limiting symbology, a systems diagram of the regulator might look like Figure 3. Resistors  $R_1$  and  $R_2$  establish the output voltage at  $[\frac{R_1 + R_2}{R_2} \times V_{REF}]$ .

Load Regulation is then  $\frac{\Delta A_{VO}/A_{VO}}{1 + \beta A_{VO}}$  where  $A_{VO}$  is the open loop gain of the error amplifier and series pass transistor and  $\beta = \frac{R_2}{R_1 + R_2}$ . Line regulation is determined by the interaction of the biasing networks with the rest of the circuit and the dominant factor is usually the stability of the voltage reference. If the reference stability is  $\Delta V_{REF}$  for a given change in input line voltage, then the overall line regulation is  $\frac{A_{VO}}{1 + \beta A_{VO}} \cdot \Delta V_{REF}$ .
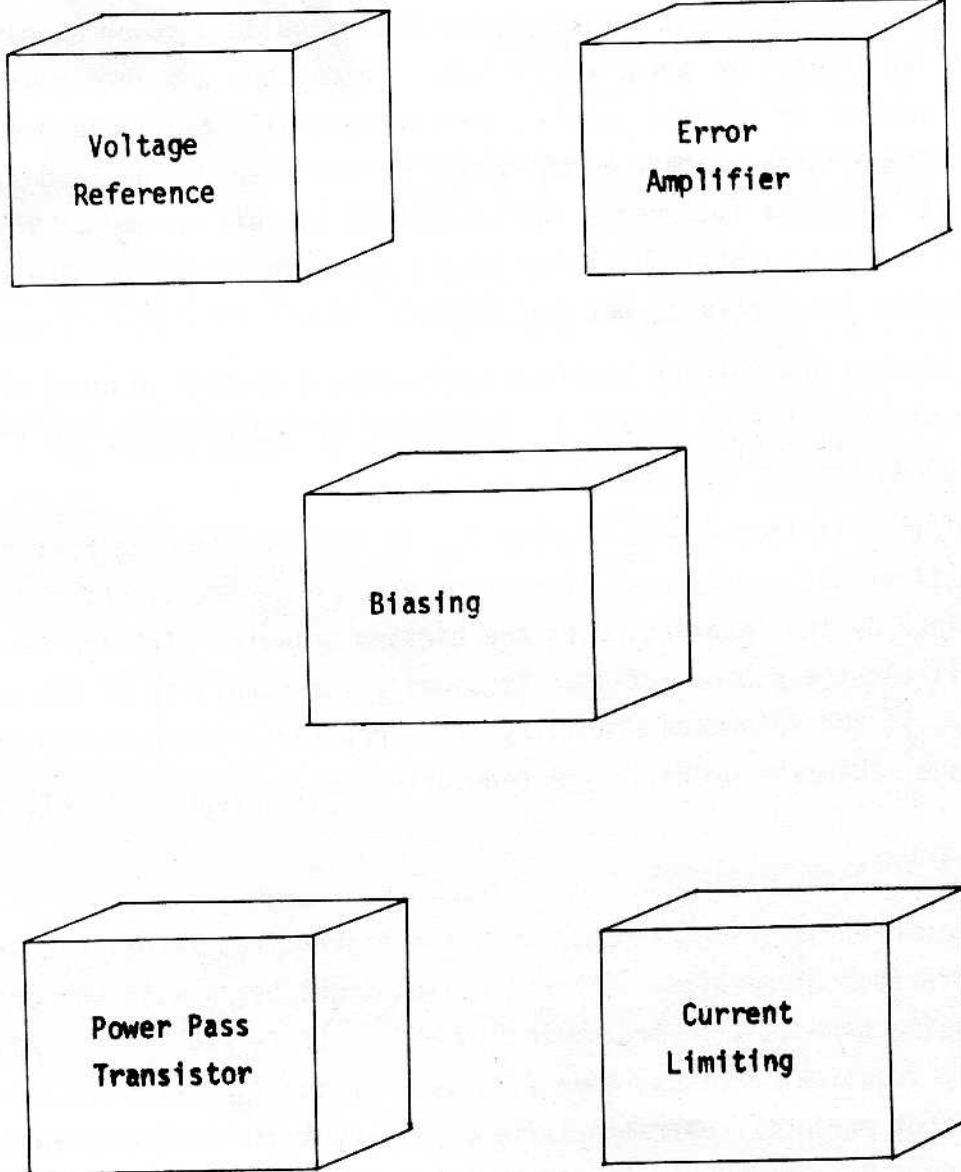
### Designing a Voltage Regulator

A lot of engineering design and common sense is required to get hardware from the previous discussion. Circuit design might begin with one or more of the biasing schemes illustrated in Figure 4. If  $T_1$  and  $T_2$  in circuit A are exactly identical devices, then  $I_1 = I_2$ . If the  $V_{BE}$  match of the two devices is not perfect, the ratio  $I_1/I_2$  will vary logarithmically with  $\Delta V_{BE}$ . Circuit B is a PNP version of A with  $I_1/I_2$  varying with the ratio of the collector areas. Temperature stability of these two circuits is poor, but an obvious advantage is their simplicity and minimum parts count.

The use of circuit C is becoming more and more popular today as FET prices decline. The tolerance in  $I_1$  is poor, but it is useful in designing circuits whose current consumption is independent of supply voltage. Without its use, minimum pre-load requirements waste several milliamps in order to



**BASIC BUILDING BLOCKS FOR VOLTAGE REGULATORS**

**FIGURE 1**



SIMPLE REGULATOR BLOCK

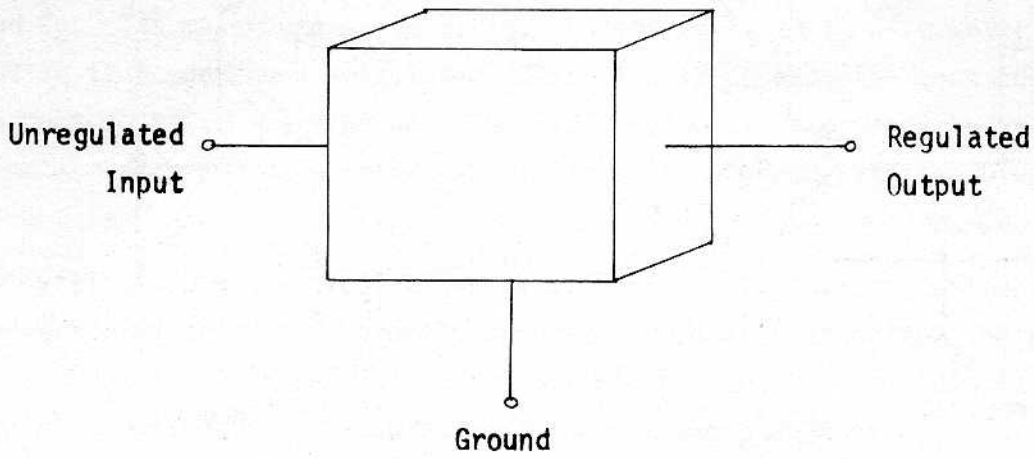


FIGURE 2

REGULATOR BLOCK DIAGRAM



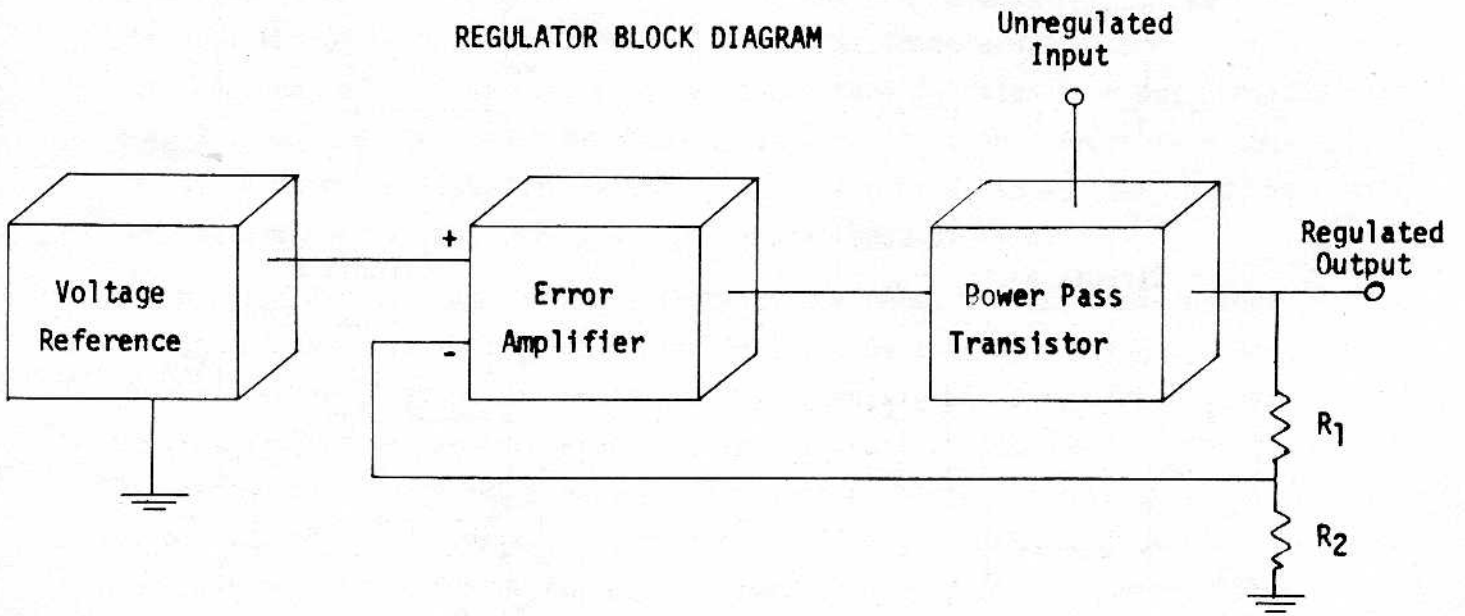


FIGURE 3


Circuit A

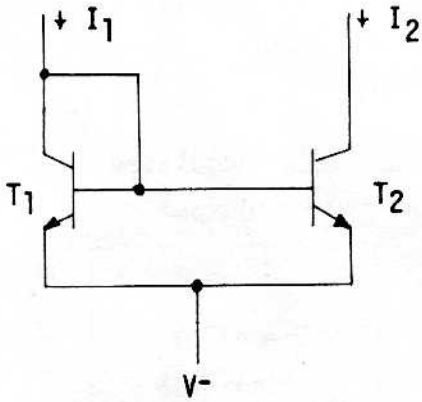


Circuit B

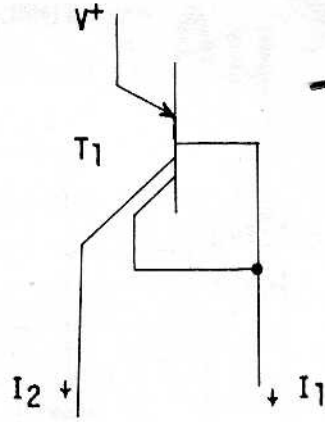


Circuit C

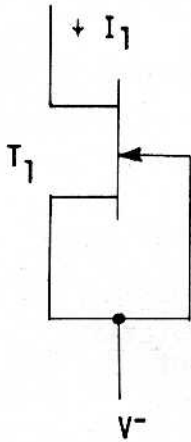

Circuit D

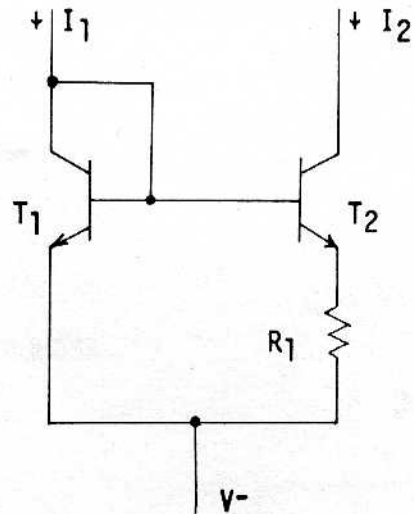

Circuit E

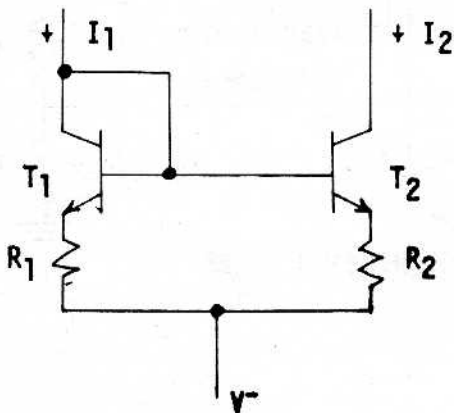

Circuit F

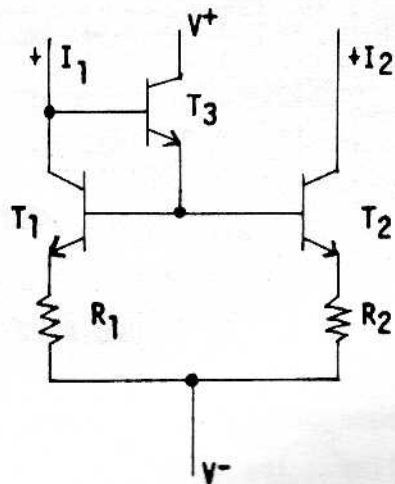


FIGURE 4

BASIC CURRENT SOURCE CONFIGURATIONS

